



G3 and G2
get shorted
here

In this case, all GNDs remain floating with respect to each other. RTN is not shorted with any of the power supply GNDs.

The difference between different GNDs (G1, G2/G3, RTN) would be kept by the power supplies driving small amounts of current through 10k resistors.

Earth GND